

## 12 Resistors in Series and Parallel, Kirchoff's Rules

### 12.1 Book Notes

For capacitors in series,

$$V_{ax} = IR_1 \quad V_{xy} = IR_2 \quad V_{yb} = IR_3 \quad (1)$$

$$V_{ab} = V_{ax} + V_{xy} + V_{yb} = I(R_1 + R_2 + R_3) \quad (2)$$

$$\frac{V_{ab}}{I} = R_1 + R_2 + R_3 \quad (3)$$

$$R_{eq} = R_1 + R_2 + R_3 \quad (4)$$

A similar argument can be made for resistors in parallel, except  $I$  is unknown, which add.

- A junction in a circuit is a point where three or more conductors meet. A loop is any closed conducting path.