

7 Capacitance, Capacitors in Series and Parallel

7.1 Book Notes

- Any two conductors separated by an insulator (or a vacuum) form a capacitor.
- Don't confuse the symbol C for capacitance (which is always in italics) with the abbreviation C for coulombs (which is never italicized).
- Thus capacitance is a measure of the ability of a capacitor to store energy.
- The reciprocal of the equivalent capacitance of a series combination equals the sum of the reciprocals of the individual capacitances.
- The magnitude of charge is the same on all plates of all the capacitors in a series combination; however, the potential differences of the individual capacitors are not the same unless their individual capacitances are the same. The potential differences of the individual capacitors add to give the total potential difference across the series combination: $V_{\text{total}} = V_1 + V_2 + V_3 + \dots$
- The equivalent capacitance of a parallel combination equals the sum of the individual capacitances.
- The potential differences are the same for all capacitors in a parallel combination; however, the charges on individual capacitors are not the same unless their individual capacitances are the same. The charges on the individual capacitors add to give the total charge on the parallel combination: $Q_{\text{total}} = Q_1 + Q_2 + Q_3 + \dots$

7.2 Recitation

- The simplest capacitor is just two plates, both with a charge $\pm Q$ (they different).
 - Capacitance, by definition, has to be positive.
 - $C = \frac{\sigma A \epsilon_0}{\sigma d} = \frac{\kappa \epsilon_0}{d}$
 - * Only depends on the geometry.
- Does example from lecture, except with sphere..
 - Except specifies direction with \hat{r}
- With series, $Q_1 = Q_2$.
 - $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$

- Opposite is true
 - $V_1 = V_2$
 - $C_{eq} = C_1 + C_2 + \dots + C_n$